

Meru university of Science and Technology
Electrical Engineering (Power Option) Level 6
ENG/CU/PO/CR/04/6
Demonstrate Understanding of Electronics
March/ April 2024

ASSESSORS INSTRUCTIONS

Ensure that all the materials and equipment are provided

The aim of the experiment is to study the working of diodes as a bridge rectifier with and without a filter capacitor

Materials required:

Transformer 12 V
Digital multimeter
Four PN diodes IN4007
One Resistor 4K Ω
One Capacitor 100 μ F
Connecting wires
Breadboard

This paper consists of 4 printed pages

Assessor should check the tool to ascertain that all the pages are printed as indicated and that no question is missing


OBSERVATION CHECKLIST

Candidate's name			
Candidates Registration number			
Assessors Name			
Unit of competency			
Date of assessment			
Items to be evaluated: <i>Tick as appropriate: YES, if the candidate performs the task correctly, NO, if the candidate did not perform the task correctly. Give a brief comment for item ticked NO).</i>	Marks available	Marks obtained	Comments
1. Adhered to prescribed safety as per workplace procedures <ul style="list-style-type: none"> • Wore PPEs (overall and safety boots). • Observed electrical safety (no loose connections at the power outlets, proper protection of the distribution board) • Observed environmental safety (waste disposal, no spills on the floor, adequate ventilation and lighting) 	3		
Task 1			
2. Identify all components required	4		
3. Listed tools used	2		
Sub-total	6		
Task 2			
4. Mounting of all components on the bread board	10		
5. Neatness	4		
Task 3			
6. Circuit operation	10		
7. Calculations to fill out table	10		
8. Waveforms <ul style="list-style-type: none"> i. Without filter ii. With filter 	10		


Grand total	63		
The candidate was found to be: Competent <input type="checkbox"/> Not yet competent <input type="checkbox"/> <i>(Please tick as appropriate)</i>			
<i>(The candidate is competent if s/he gets 9(65%) of the 11 items on the observation checklist.)</i>			
Feedback from candidate:			
Feedback to candidate:			
Candidate's signature:	Date:		
Assessor's signature:	Date:		

Comments by Assessor:


WITHOUT FILTER A

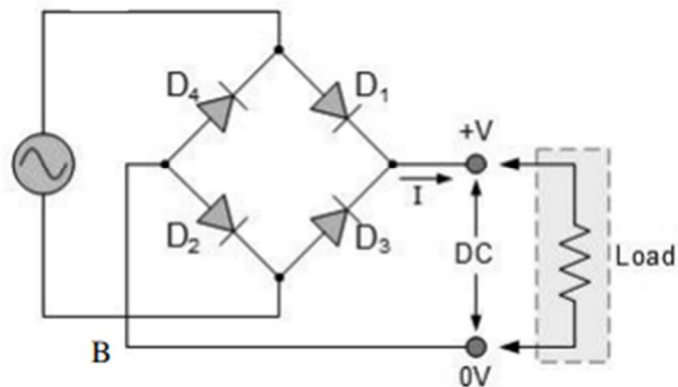


WITH FILTER:

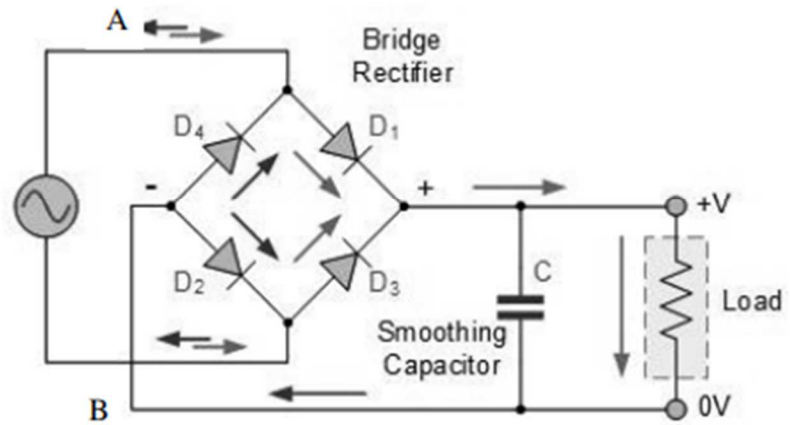

Expected waveforms

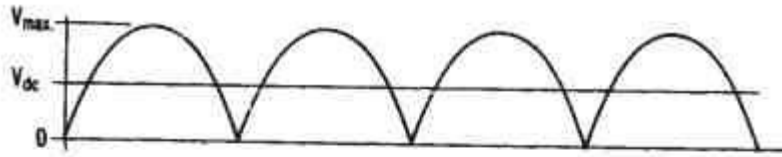

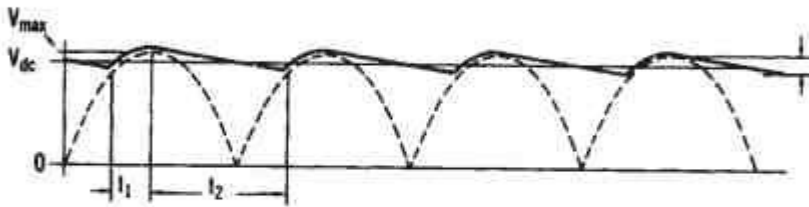(B) Full-wave output waveform with no filter capacitor.



(C) Full-wave output waveform with filter capacitor across load.

